

### 1. Introduction

Some applications, such as voice computer telephony, require higher power transmission from the host equipment to the telephone network. This application note describes changes to the standard LITELINK II application circuits to provide the transmit gain needed for a particular application.

Note: The recommended maximum drive level into the line from LITELINK II is 6 mA peak, which is equivalent to about +10 dBm into a 600 Ω load. Datasheet specifications for maximum current ( $I_{DDL}$ ) do not apply with higher than specified output power. LITELINK II will draw more current with higher output power.

### 2. Transmit Gain Design Procedure

1. Determine the peak transmit level needed for the application.
2. If necessary, convert the required peak transmit power into a voltage level. For example, 0 dBm into 600 Ω = 1.1 V<sub>P</sub>
3. Calculate the required linear voltage gain  $A_V$  by dividing the peak transmit voltage level from step 2 by 1.1.
4. Modify the following application circuit component values:

$$Z_{ZTX} \leftarrow Z_{ZTX} / A_V$$

$$Z_{ZNT} \leftarrow Z_{ZNT} / A_V$$

$$R_{NTF} \leftarrow \frac{R_{NTF}}{((A_V - 1)(R_{NTF} / R_{NTS}) + A_V)}$$

These calculations result in a transmit (4-wire to 2-wire) gain of  $A_V$ , and a receive gain (2-wire to 4-wire) of  $1/A_V$ . If necessary, the receive loss can be compensated with either the programmable input gain of a CODEC or with a discrete op-amp gain stage between the LITELINK RX output and the host system.

### 3. Examples

#### 3.1 PBX Example

To meet +3.18 dBm into 900 Ω, use the following calculations:

$$+3.18 \text{ dBm into } 900 \text{ } \Omega = 1.935 \text{ V}_P$$

$$1.935 \text{ V} / 1.1 \text{ V} = 1.76.$$

The calculations work out as follows:

$$R_{ZTX} = 226 / 1.76 = 128.4$$

$$R_{ZNT} = 453 / 1.76 = 257.0$$

$$R_{NTF} = 1M / 2.53 = 396683$$

The closest standard resistor values are 127 Ω for  $R_{ZTX}$ , 255 Ω for  $R_{ZNT}$ , and 392 kΩ for  $R_{NTF}$ .

#### 3.2 +3 dBm into 600 Ohm Transmit Power Example

The following application circuit uses component values determined by the design procedure above for +3 dBm transmit power into 600 Ω.

Peak transmit power of +3 dBm into 600 Ω = 1.55 V<sub>P</sub>  
 $1.55 / 1.1 = 1.41$ . The calculations work out as follows:


$$R_{ZTX} = 150 / 1.41 = 106.4$$

$$R_{ZNT} = 301 / 1.41 = 213.5$$

$$R_{NTF} = 1M / 1.82 = 549000$$

Standard resistor values have been substituted in the circuit in Figure 1.

Figure 1. +3 dBm Application Circuit

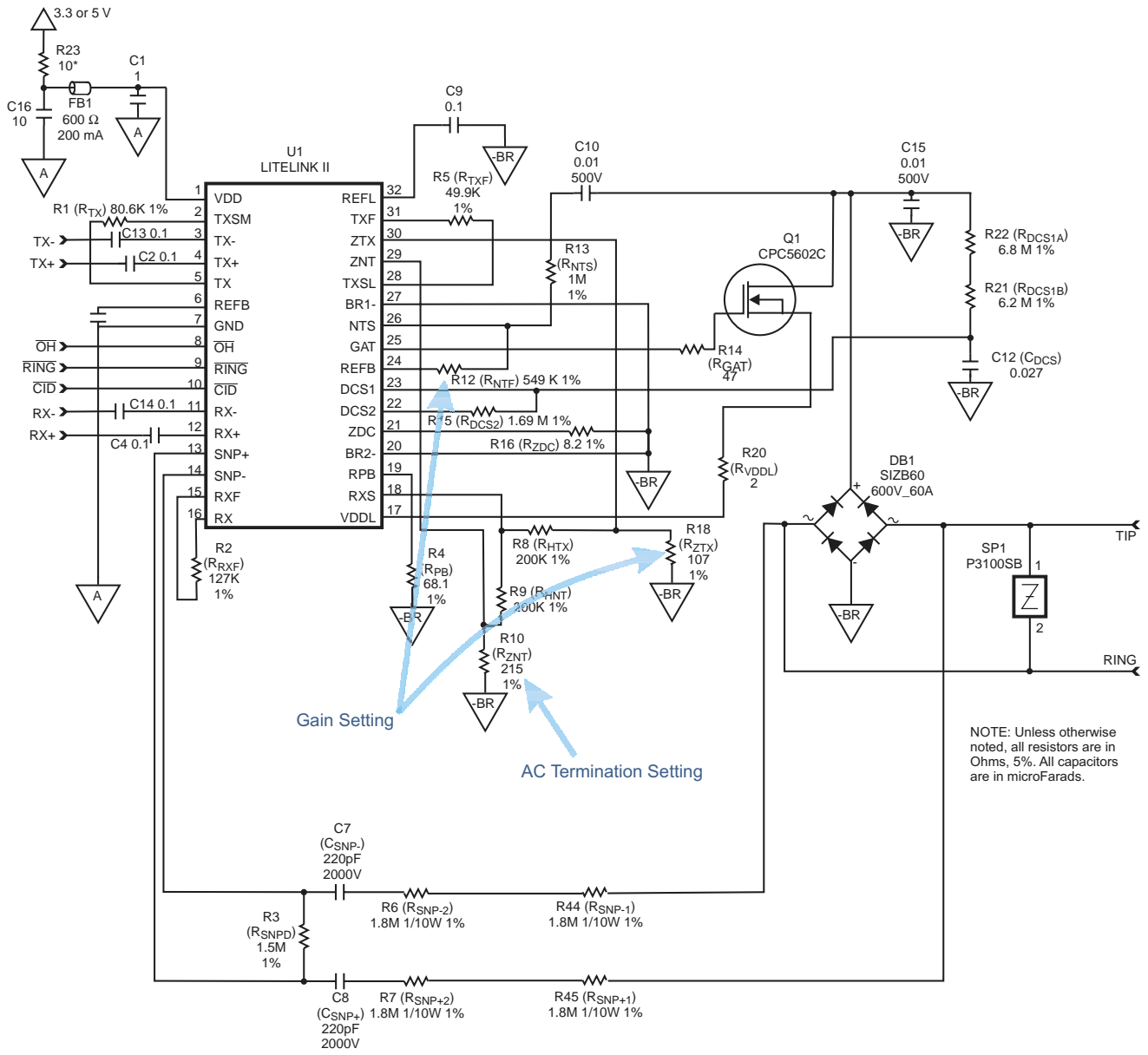



## 4. LITELINK Design Resources

### 4.1 Clare, Inc. Design Resources

The Clare, Inc. web site has a wealth of information useful for designing with LITELINK, including application notes and reference designs that already meet all applicable regulatory requirements. LITELINK data sheets also contains additional application and design information. See the following links:

#### LITELINK datasheets and reference designs

Application note AN-107 [LOCxx Series - Isolated Amplifier Design Principles](#)

Application note AN-114 [ITC117P](#)

Application note AN-117 [Customize Caller-ID Gain and Ring Detect Voltage Threshold for CPC5610/11](#)

Application note AN-140, [Understanding LITELINK](#)

Application note AN-141, [Enhanced Pulse Dialing with LITELINK](#)

Application note AN-143, [Loop Reversal Detection with LITELINK](#)

Application note AN-146, [Guidelines for Effective LITELINK Designs](#)

Application note AN-147, [Worldwide Application of LITELINK](#)

Application note AN-150, [Ground-start Supervision Circuit Using IAA110](#)

### 4.2 Third Party Design Resources

The following also contain information useful for DAA designs. All of the books are available on [amazon.com](#).

*Understanding Telephone Electronics*, Stephen J. Bigelow, et. al., Butterworth-Heinemann; ISBN: 0750671750

*Newton's Telecom Dictionary*, Harry Newton, CMP Books; ISBN: 1578200695

*Photodiode Amplifiers: Op Amp Solutions*, Jerald Graeme, McGraw-Hill Professional Publishing; ISBN: 007024247X

[Teccor, Inc. Surge Protection Products](#)

*United States Code of Federal Regulations*, CFR 47 Part 68.3

---

### For additional information please visit [www.clare.com](http://www.clare.com)

*Clare, Inc. makes no representations or warranties with respect to the accuracy or completeness of the contents of this publication and reserves the right to make changes to specifications and product descriptions at any time without notice. Neither circuit patent licenses or indemnity are expressed or implied. Except as set forth in Clare's Standard Terms and Conditions of Sale, Clare, Inc. assumes no liability whatsoever, and disclaims any express or implied warranty relating to its products, including, but not limited to, the implied warranty of merchantability, fitness for a particular purpose, or infringement of any intellectual property right.*

*The products described in this document are not designed, intended, authorized, or warranted for use as components in systems intended for surgical implant into the body, or in other applications intended to support or sustain life, or where malfunction of Clare's product may result in direct physical harm, injury, or death to a person or severe property or environmental damage. Clare, Inc. reserves the right to discontinue or make changes to its products at any time without notice.*